
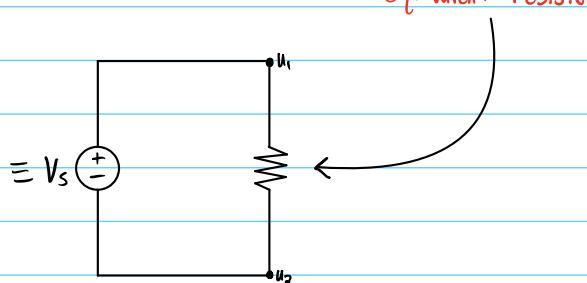


Discussion 8B !!


Resistor Equivalence:

Main Idea → Simplify circuits in order to ease circuit analysis and computations

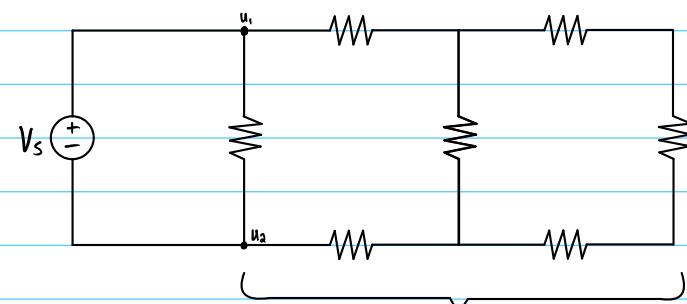Example: complex resistor network → simple circuit




Resistor Equivalence

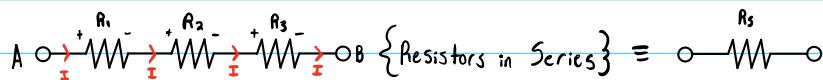

I → Some current flowing through each resistor

$$R_s = R_1 + R_2 + R_3$$

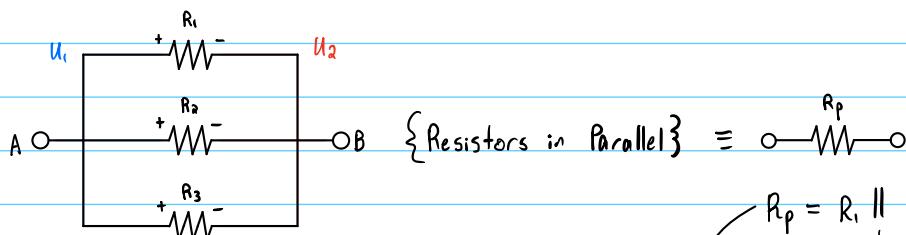

Same voltage drop across each resistor
 $(u_1 - u_2)$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$R_p = R_1 \parallel R_2 \parallel R_3$
 ↴ "parallel operator"

Superposition:

Motivation: Break down circuits with multiple sources into several simpler circuits
↳ another tool for circuit analysis


Steps:

- ① Identify each independent current/voltage source within the circuit




- ② For each source identified in step ①, draw an equivalent circuit by zeroing out all other independent sources.

Zeroing out a Voltage Source:

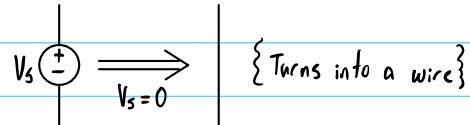

Zeroing out a Current Source:

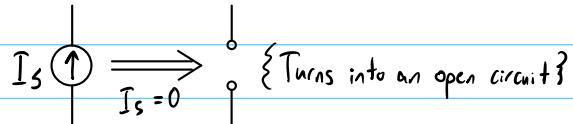




- ③ Compute the circuit voltages and currents due to the independent source you are working with (This is the largest step and will be repeated several times).

- ④ Finally, Superimpose the individual circuits by adding up the currents and node potentials that directly correspond to each other.

1. Superposition

For the following circuits, use the superposition theorem to solve for the voltages across the resistor(s).

(a)

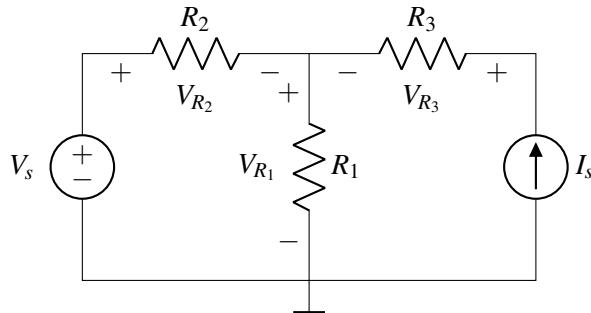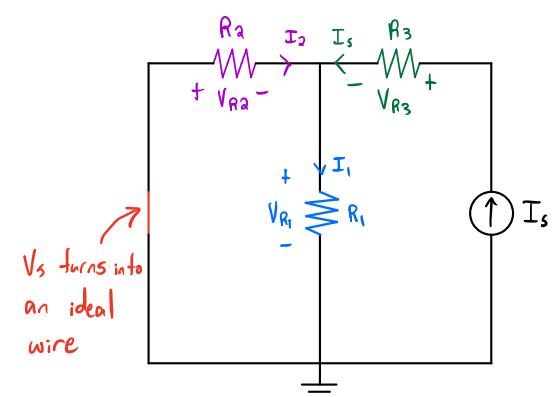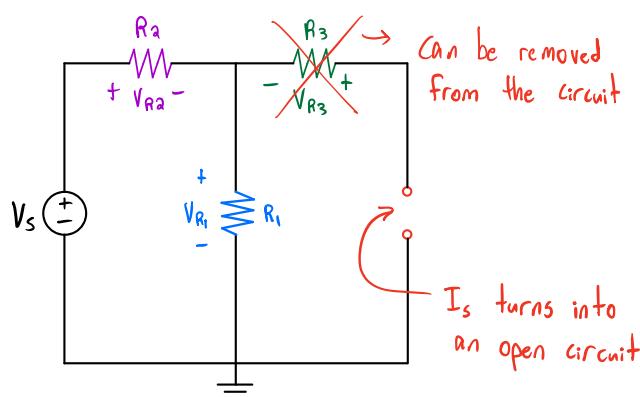Zeroing I_s Zeroing V_s 

The circuit reduces to a voltage divider!

$$V_{R_1} = \frac{R_1}{R_1 + R_2} V_s$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_s$$

$$V_{R_3} = 0$$

$$V_{R_3} = I_s R_3 \quad (R_3 \text{ is in series with } I_s)$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_s \quad (\text{Current Divider})$$

$$V_{R_1} = -V_{R_2} \quad (\text{Parallel resistors with opposite polarity})$$

$$I_2 = -\frac{R_1}{R_1 + R_2} I_s$$

$$V_{R_1} = I_1 R_1 \quad (\text{By Ohm's Law})$$

$$V_{R_1} = \frac{R_1 R_2}{R_1 + R_2} I_s$$

$$V_{R_2} = -\frac{R_1 R_2}{R_1 + R_2} I_s$$


Finally, we superimpose the individual contributions from V_s and I_s to get:

$$V_{R_1} = \frac{R_1}{R_1 + R_2} V_s + V_{R_1} = \frac{R_1 R_2}{R_1 + R_2} I_s$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_s - \frac{R_1 R_2}{R_1 + R_2} I_s$$

$$V_{R_3} = 0 + I_s R_3 = I_s R_3$$


(b)

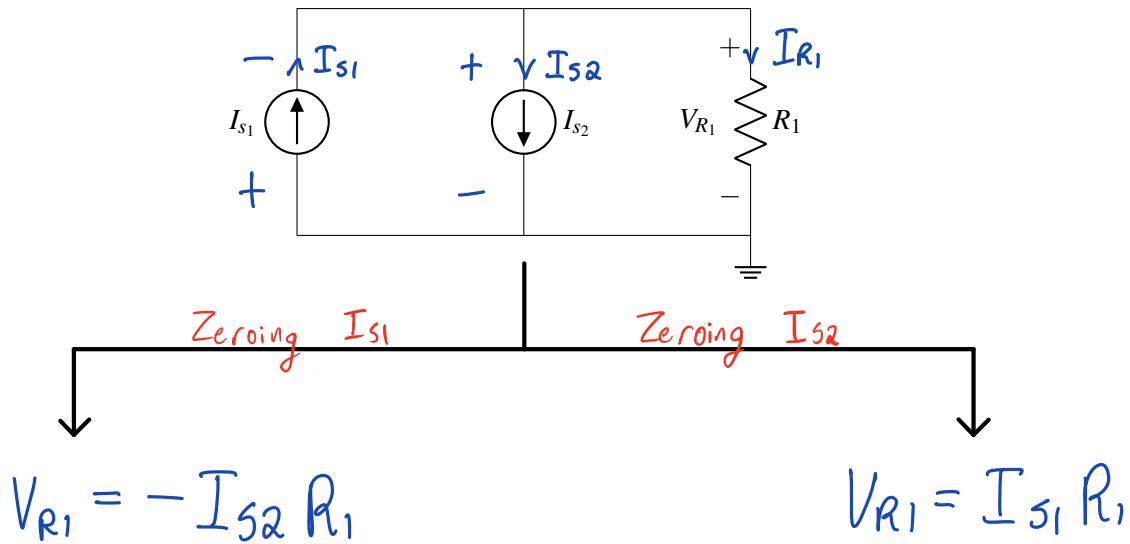


$$V_{R1} = -I_{s2} R_1 + I_{s1} R_1$$

$$V_{R1} = R_1 (I_{s1} - I_{s2})$$

(c) (PRACTICE)

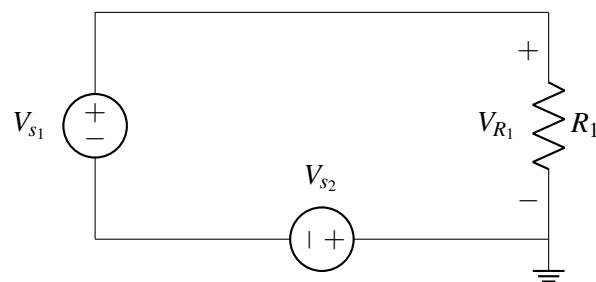

Thevenin Equivalent:

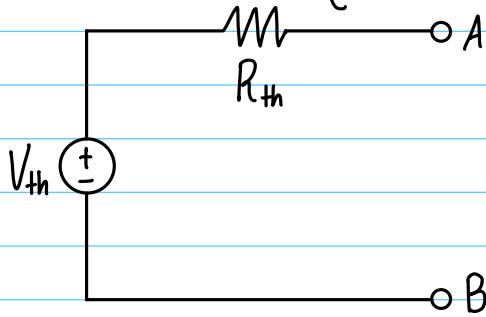

To Solve:


- ① Find V_{th} by finding V_{AB} in given circuit

$$V_{th} = V_{AB} \quad \text{open circuit voltage}$$

- ② Zero out all independent sources and apply a test current I_{test} through the terminal or V_{test} across it

$$R_{th} = \frac{V_{test}}{I_{test}}$$

Thevenin Equivalent:

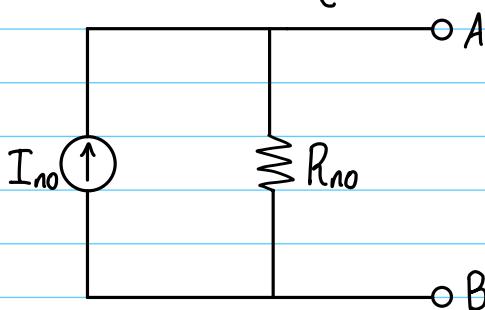

To Solve:

- ① Find I_{no} by finding I_{AB} in given circuit

$$I_{no} = I_{sc} \quad \text{short circuit current}$$

- ② Zero out all independent sources and apply a test current I_{test} through the terminal or V_{test} across it

$$R_{th} = \frac{V_{test}}{I_{test}}$$


Note: $R_{th} = R_{no}$

Why do we care?

- We can reduce large, complex circuits to their Thevenin and Norton equivalent with the same output behavior
- saves space, time, money, etc.
- Drawback: you lose intermediate information

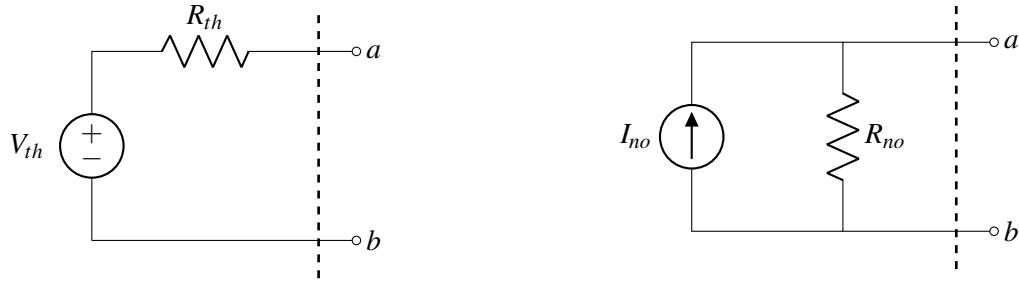
2. Thevenin and Norton Equivalence

The general Thévenin and Norton equivalent circuits are shown below:



Find the Thévenin and Norton equivalents across terminals a and b for the circuits given below.


(a)

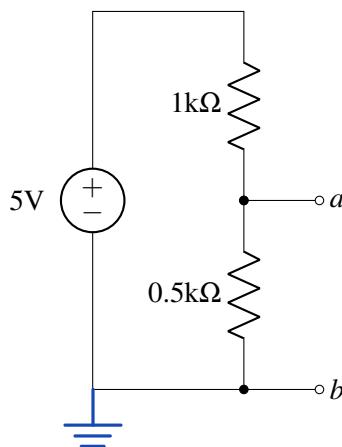

Voltage Divider!

$$V_{ab} = U_a - U_b = U_a - 0 = U_a = \frac{0.5\text{k}\Omega}{1\text{k}\Omega + 0.5\text{k}\Omega} \cdot 5\text{V} = 1.67\text{V}$$

To find R_{th} , we must zero out V_s :

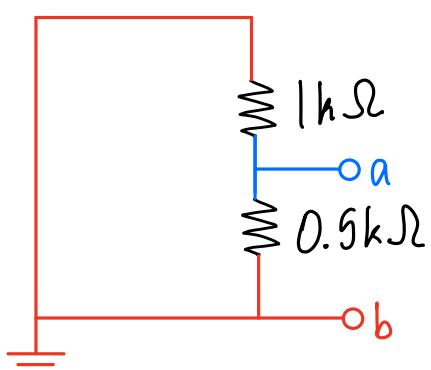


$$R_{th} = 1\text{k}\Omega \parallel 0.5\text{k}\Omega$$

$$R_{th} = \frac{1\text{k}\Omega \cdot 0.5\text{k}\Omega}{1\text{k}\Omega + 0.5\text{k}\Omega} = 333\text{\Omega}$$


Since $R_{th} = R_{no}$,

$$I_{no} = \frac{V_{th}}{R_{th}} = \frac{1.67\text{V}}{333\text{\Omega}} = 5\text{A}$$

(b)

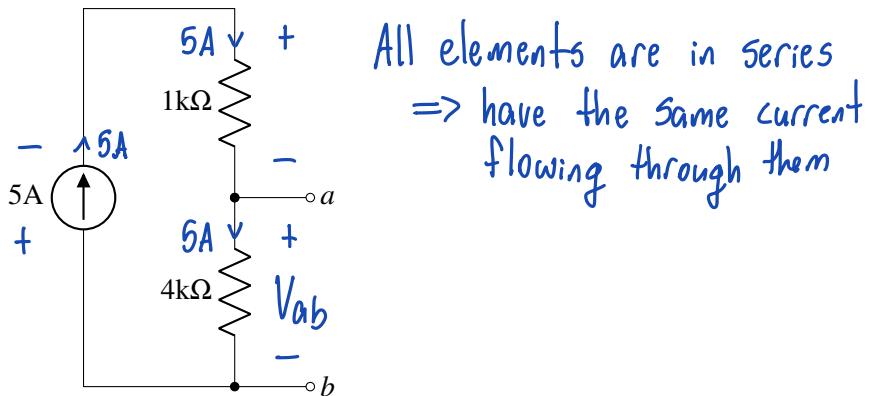
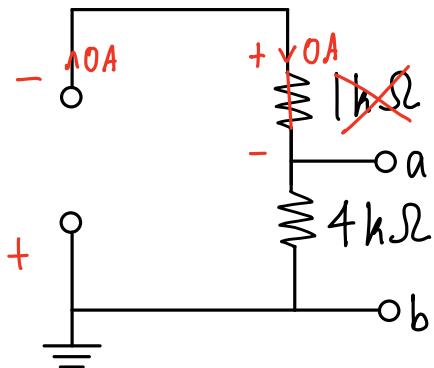
$$\text{By Ohm's Law, } V_{th} = V_{ab} = 5A \cdot 4k\Omega = 20kV$$




$$R_{th} = 4k\Omega$$


$$I_{no} = \frac{V_{th}}{R_{th}} = \frac{20kV}{4k\Omega} = 5A$$

Simplified Circuits:

Thevenin

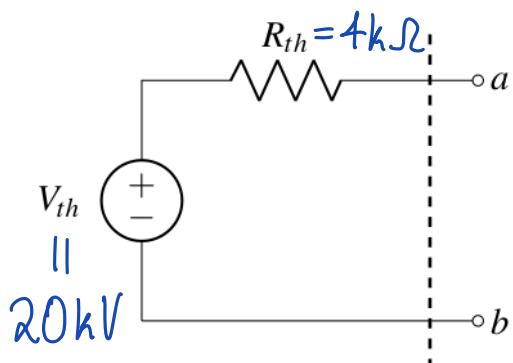

Norton

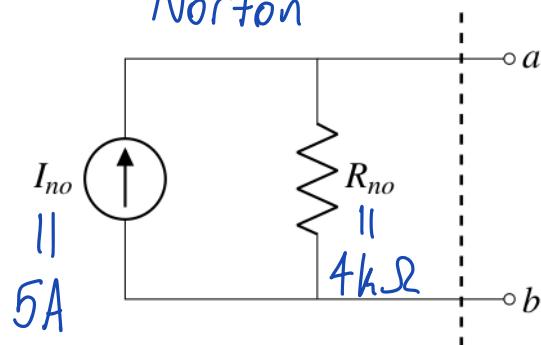

tinyurl.com/16Anish

Password: integrity